

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**NOIDA INSTITUTE OF ENGINEERING AND TECHNOLOGY, GREATER NOIDA**

(An Autonomous Institute Affiliated to AKTU, Lucknow)

**B. Tech**

**SEM: III - THEORY EXAMINATION - (2023 - 2024)**

**Subject: Digital Logic & Circuit Design**

**Time: 3 Hours**

**Max. Marks: 100**

**General Instructions:**

**IMP:** Verify that you have received the question paper with the correct course, code, branch etc.

1. This Question paper comprises of **three Sections -A, B, & C**. It consists of Multiple Choice Questions (MCQ's) & Subjective type questions.
2. Maximum marks for each question are indicated on right -hand side of each question.
3. Illustrate your answers with neat sketches wherever necessary.
4. Assume suitable data if necessary.
5. Preferably, write the answers in sequential order.
6. No sheet should be left blank. Any written material after a blank sheet will not be evaluated/checked.

**SECTION-A**

20

1. Attempt all parts:-

- 1-a. 1's complement of Binary number 101010 is \_\_\_\_\_. (CO1) 1
- (a) 10101
  - (b) 11011
  - (c) 1000
  - (d) 101011
- 1-b. \_\_\_\_\_ is called Universal Gate.(CO1) 1
- (a) XOR Gate
  - (b) XNOR Gate
  - (c) NAND Gate
  - (d) AND Gate
- 1-c. A half adder circuit has two inputs and (CO2) 1
- (a) one output
  - (b) two output
  - (c) three output
  - (d) none of these
- 1-d. If there are n selection lines, then the number of maximum possible input lines is \_\_\_\_\_ . (CO2) 1
- (a)  $2^n$
  - (b) n

- (c)  $2n$   
 (d)  $n/2$
- 1-e. The basic latch consists of \_\_\_\_\_ (CO3) 1  
 (a) Two inverters  
 (b) Two comparators  
 (c) Two amplifiers  
 (d) Two adders
- 1-f. Number of flip-flops required in MOD 5 counter. (CO3) 1  
 (a) 2  
 (b) 3  
 (c) 4  
 (d) 5
- 1-g. How many flip-flops are required to construct a decade counter? (CO4) 1  
 (a) 4  
 (b) 8  
 (c) 5  
 (d) 10
- 1-h. In which model, the next state is a function of the present state and the present inputs. Its output is also a function of the present state and the present inputs. (CO4) 1  
 (a) Mealy Circuit model  
 (b) Moore Circuit Model  
 (c) Both of these  
 (d) None of these
- 1-i. The full form of ROM is \_\_\_\_\_ (CO5) 1  
 (a) Read Outside Memory  
 (b) Read Out Memory  
 (c) Read Only Memory  
 (d) Read One Memory
- 1-j. PLDs with programmable AND and fixed OR arrays are called \_\_\_\_\_ (CO5) 1  
 (a) PAL  
 (b) PLA  
 (c) APL  
 (d) PPL

2. Attempt all parts:-

- 2.a. List out the truth table entry for two input NAND Gate.(CO1) 2  
 2.b. Define Multiplexer. (CO2) 2

- 2.c. Differentiate between edge triggering and level triggering. (CO3) 2
- 2.d. Define propagation delay time. (CO4) 2
- 2.e. Differentiate between ROM and RAM. (CO5) 2

### **SECTION-B**

30

3. Answer any five of the following:-

- 3-a. Construct the Hamming code for the 4 bit data 1010. Consider the even parity. (CO1) 6
- 3-b. Implement the Boolean expression  $F(A,B,C) = ABC' + A'B' + AC'$  using both universal logic gates. (CO1) 6
- 3-c. Implement the SUM and CARRY Boolean functions of full adder using multiplexers. (CO2) 6
- 3-d. What is the logic implementation of half adder? Implement full adder using half adders. (CO2) 6
- 3.e. What is a master-slave flip-flop? Explain its working with suitable diagram. (CO3) 6
- 3.f. Difference between synchronous and asynchronous sequential circuits. (CO4) 6
- 3.g. Differentiate and compare FPGA and CPLD. (CO5) 6

### **SECTION-C**

50

4. Answer any one of the following:-

- 4-a. Minimize the given four variable logic function using Quine Mc-Clusky Method:- (CO1) 10  
 $F(A, B, C, D) = \sum m(0,1, 2, 3,5, 7, 8, 9, 11, 14)$
- 4-b. Simplify the logic expression using K map:- (CO1) 10  
 $F(A, B, C, D, E) = \sum m(0, 5, 6, 8, 9, 10, 11, 16, 20, 24, 25, 26, 27, 29, 31)$

5. Answer any one of the following:-


- 5-a. Design a combinational circuit that will compare two 4-bit numbers. (CO2) 10
- 5-b. Design a combinational circuit that accepts a three-bit number and generates an output binary number equal to the square of the input number. (CO2) 10

6. Answer any one of the following:-

- 6-a. What is a flip-flop? Convert SR flip flop to D flip flop. (CO3) 10
- 6-b. Explain universal shift register in detail. (CO3) 10

 7. Answer any one of the following:-

- 7-a. Explain Hazards in sequential circuits. (CO4) 10
- 7-b. Draw the reduced state table and reduce state diagram for the state diagram shown in fig. (CO4) 10



8. Answer any one of the following:-

8-a. Implement the following functions using PLA (CO5)

10

i)  $A(x,y,z) = \sum m(1,2,4,6)$

ii)  $B(x,y,z) = \sum m(0,1,6,7)$

iii)  $C(x,y,z) = \sum m(2,6)$

8-b. Compare various programmable devices. (CO5)

10

COP. JULY 2024