



(d) the emitter

- 1-d. What is the value of drain current in JFET when  $V_{gs}$ =pinch off voltage? (CO4) 1
- (a) 0A
  - (b) 1A
  - (c) 2A
  - (d) Cannot be determined
- 1-e. An oscillator produces..... oscillations (CO5) 1
- (a) Damped
  - (b) Undamped
  - (c) Modulated
  - (d) None of the above

2. Attempt all parts:-

- 2.a. Define the term mobility with reference to semiconductor materials. (CO1) 2
- 2.b. Define PIV for HWR and FWR. (CO2) 2
- 2.c. Why CE configuration is most preferred configuration?(CO3) 2
- 2.d. Define logic gates. Give the symbol representation of all gates. (CO4) 2
- 2.e. Define slew rate. (CO5) 2

## SECTION B

15

3. Answer any three of the following:-

- 3-a. With neat and clean energy band diagram classify conductors , semiconductors and Insulators. (CO1) 5
- 3-b. What are the effect of temperature on the V-I characteristics of diode? Draw and explain the observations of V-I characteristics of Si for 4 different temperatures. (CO2) 5
- 3.c. Draw and explain the input and output characteristics of common emitter (CE) configuration using NPN bipolar junction transistor. Also indicate all the the region of operations. (CO3) 5
- 3.d. What is counter? Explain the working of synchronous counter with neat and clean circuit diagram. (CO4) 5
- 3.e. Draw the differentiator circuit and derive the expression for the output voltage. Also draw the input and output voltage waveforms. (CO5) 5

## SECTION C

20

4. Answer any one of the following:-

- 4-a. Explain the formation of Depletion layer. (CO1) 4
- 4-b. Explain Energy band theory of Solids and draw energy band diagram showing how energy band separated in solids. (CO1) 4
5. Answer any one of the following:-
- 5-a. Define diffusion current and Drift current in a semiconductor in details. Also write current equations.(CO2) 4
- 5-b. For the same order of doping, why does n-type semiconductor exhibit larger conductivity than p-type semiconductor? Also explain why Si is most widely used semiconductor? (CO2) 4
6. Answer any one of the following:-
- 6-a. Draw and explain the input and output characteristics of common base configuration. (CO3) 4
- 6-b. Explain the factors affecting the stability of Q point.(CO3) 4
7. Answer any one of the following:-
- 7-a. Explain the Working and Characteristics of Enhancement Type N-MOSFET (CO4) 4
- 7-b. What is demultiplexer? What are the applications of demultiplexer (DMUX)? (CO4) 4
8. Answer any one of the following:-
- 8-a. What are advantages of negative feedback? Explain the different types of feedback topologies. (CO5) 4
- 8-b. Define ideal op-amp and write its ideal and practical characteristics. (CO5) 4