

- (d) 5
- 1-d. Power dissipation in switch logic is (CO4) 1
- (a) less
 - (b) more
 - (c) high
 - (d) very less
- 1-e. In negative logic convention, the Boolean Logic [1] is equivalent to: (CO5) 1
- (a) +VDD
 - (b) 0 V
 - (c) -VDD
 - (d) None of the mentioned

2. Attempt all parts:-

- 2.a. What is W/ L ratio? (CO1) 2
- 2.b. What is static power dissipation in CMOS? (CO2) 2
- 2.c. What is Gray Code? (CO3) 2
- 2.d. What is the basis of power consumption in VLSI circuit? (CO4) 2
- 2.e. How the propagation delay get affected by increasing fanout? (CO5) 2

SECTION B

20

3. Answer any five of the following:-

- 3-a. Draw the fabrication steps of NMOS transistor and explain its operation in detail. (CO1) 4
- 3-b. Why PMOS transistor size is double the size of NMOS transistor? (CO1) 4
- 3-c. Write short notes on gate oxide thickness. (CO2) 4
- 3-d. Explain Threshold voltage in CMOS, write it's importance. (CO2) 4
- 3.e. Write the Excitation table and characteristic equation of T flip flop. (CO3) 4
- 3.f. What are the objectives of performance management? (CO4) 4
- 3.g. What is multiplexer? Explain with the help of circuit diagram. (CO5) 4

SECTION C

35

4. Answer any one of the following:-

- 4-a. Explain parasitic capacitance with the help of diagram. (CO1) 7
- 4-b. How can leakage current be reduced in CMOS? Explain with circuit diagram. (CO1) 7

5. Answer any one of the following:-

- 5-a. Explain probabilistic power estimation approaches. (CO2) 7
- 5-b. What are the 5 steps of a simulation? Explain in detail. (CO2) 7

6. Answer any one of the following:-

- 6-a. Explain briefly the difference between the Mealy model and Moore model. (CO3) 7
- 6-b. What are the differences between synchronous and asynchronous counter? (CO3) 7

7. Answer any one of the following:-

- 7-a. What is Flow Graph Transformation? Explain in details. (CO4) 7
- 7-b. What is adaptive performance management? Explain. (CO4) 7

8. Answer any one of the following:-

- 8-a. What is CMOS? Implement CMOS circuit of given boolean expression $Y=(ab+c+d)'$. (CO5) 7
- 8-b. What do you mean by Package Co-design of clock network? Explain. (CO5) 7

REG. MAY 2024