





Q.No	Question Content	Question Image	Category	Sub Category	Marks	Options Randomization	Type	Difficulty	Correct	Option1	Option2	Option3	Option4
35	For a non-inverting Amplifier, voltage gain is _____.		Attempt All Questions	4 X 2 = 8	2		Single Choice	Smart					